



BTECH
(SEM IV) THEORY EXAMINATION 2024-25
NETWORKS ANALYSIS & SYNTHESIS

TIME: 3 HRS

M.MARKS: 70

Note: Attempt all Sections. In case of any missing data; choose suitably.

SECTION A

1. Attempt all questions in brief. 02 x 7 = 14

Q no.	Question	CO	Level
a.	Define Link and co-tree.	1	K2
b.	State reciprocity theorem.	2	K2
c.	Differentiate between natural response and force response.	3	K2
d.	Derive condition for maximum power transfer.	2	K2
e.	State the compensation theorem.	2	K2
f.	Discuss the properties of RC driving point function.	4	K2
g.	Differentiate between active filter and passive filter.	5	K2

SECTION B

2. Attempt any three of the following: 07 x 3 = 21

Q no.	Question	CO	Level
a.	<p>Write the incidence matrix and cut-set matrix for the network shown in figure.</p>	1	K2
b.	<p>Find V_0 using the superposition theorem.</p>	2	K3
c.	<p>A constant voltage of 100V is applied at $t = 0$ to a RC series circuit having $R = 5M\Omega$, $C = 20\mu F$. Assuming no initial charge to the capacitor, find current i and the voltage across R and C.</p>	3	K3
d.	<p>Find the z-parameter of the given network shown in figure.</p>	4	K3
e.	<p>Design a constant K type low pass filter of 2000Hz and a zero-frequency characteristics impedance of 200Ω. Draw T and π section of the filter.</p>	5	K4



BTECH
(SEM IV) THEORY EXAMINATION 2024-25
NETWORKS ANALYSIS & SYNTHESIS



TIME: 3 HRS

M.MARKS: 70

SECTION C



3. Attempt any *one* part of the following:

$$07 \times 1 = 07$$

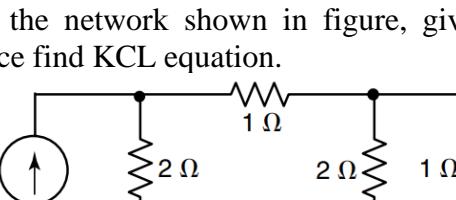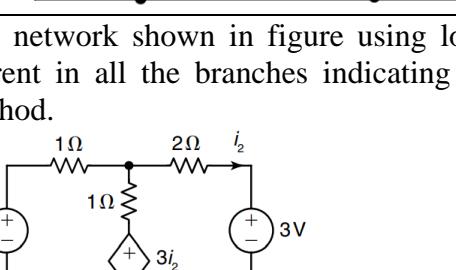Q no.	Question	CO	Level
a.	<p>For the network shown in figure, give fundamental cut-set matrix and hence find KCL equation.</p> 	1	K3
b.	<p>The network shown in figure using loop method of analysis, determine current in all the branches indicating their directions, use graph theory method.</p> 	1	K3

4. Attempt any *one* part of the following:

$$07 \times 1 = 07$$

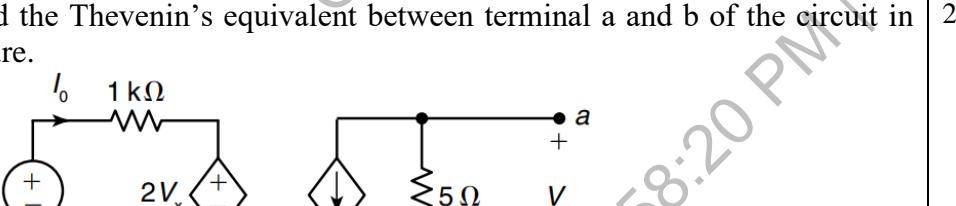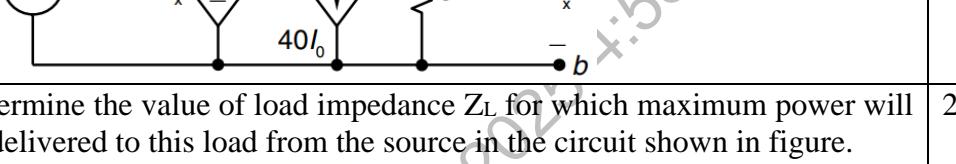Q no.	Question	CO	Level
a.	<p>Find the Thevenin's equivalent between terminal a and b of the circuit in figure.</p> 	2	K3
b.	<p>Determine the value of load impedance Z_L for which maximum power will be delivered to this load from the source in the circuit shown in figure.</p> 	2	K3

5. Attempt any *one* part of the following:


$$07 \times 1 = 07$$


Q no.	Question	CO	Level
a.	In given circuit shown, switch is closed at $t=0$. Find the current in the circuit at any time t using Laplace transform.	3	K2

BTECH
(SEM IV) THEORY EXAMINATION 2024-25
NETWORKS ANALYSIS & SYNTHESIS

TIME: 3 HRS



M.MARKS: 70

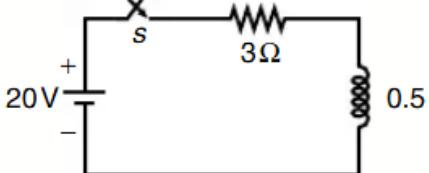			
b.	The circuit shown in figure consist of resistance, inductance and capacitance in series with 100V constant source. When the switch is closed $t=0$, find the transient current.	3	K3

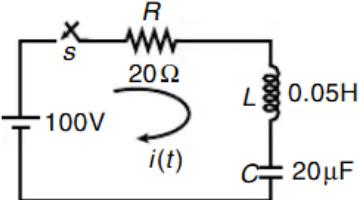

6. Attempt any one part of the following:

07 x 1 = 07

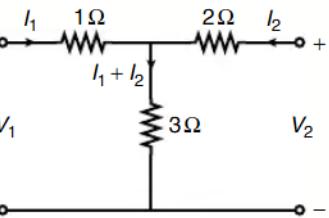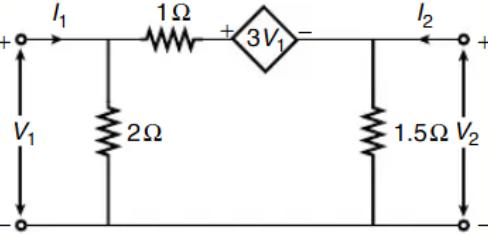Q no.	Question	CO	Level
a.	Find transmission parameter of network in figure. Further prove that $AD - BC = 1$	4	K3
			
b.	Determine the Y- Parameter for the network shown in figure.	4	K3
			

7. Attempt any one part of the following:

07 x 1 = 07

Q no.	Question	CO	Level
a.	Test whether the following polynomial is Hurwitz or not. $F(s) = \frac{2s^4 + 6s^3 + 11s^2 + 10s + 5}{s^4 + 5s^3 + 8s^2 + 9s + 6}$	5	K4
b.	Find Cauer form -I and Cauer form -II of the following $Z(s) = \frac{s(s^2 + 3)(s^2 + 5)}{(s^2 + 2)(s^2 + 4)}$	5	K4